

### 4.3 A Second-Order Multiple-Feedback Band-Pass Filter

Another circuit which realizes the second-order band-pass filter is the multiple-feedback network [21] shown in Fig. 4.4. Analysis shows that it realizes Eq. (4.1) for the values

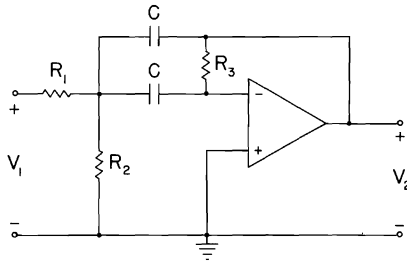


Fig. 4.4. A multiple-feedback second-order band-pass filter.

$$B = \frac{2}{R_3 C}$$

$$\omega_0^2 = \frac{1}{R_3 C^2} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) \quad (4.4)$$

The constant  $K$  in Eq. (4.1) is given by  $-1/R_1 C$ , and hence the circuit yields an inverting gain (negative) with magnitude  $R_3/2R_1$ . This may be converted to a noninverting gain, if one wishes, by cascading Fig. 4.4 with an inverting amplifier.

For high  $Q$ , the network of Fig. 4.4 has a wide spread of element values and large  $Q$  sensitivities. For this reason it should probably be restricted to values of  $Q \leq 10$ . The network has the nice feature that one may specify  $f_0$ ,  $Q$ , and the gain. Practical values of the capacitances and resistances may be obtained using the procedure described in the summary at the end of the chapter.

As an example, let  $f_0 = 1000$  Hz,  $Q = 10$ , and gain = 10. From Fig. 4.11*b*, we have a  $K$  parameter of 10, and from Fig. 4.31, we have  $R_1 = 15.9$  k $\Omega$ ,  $R_2 = 840$   $\Omega$ ,  $R_3 = 318$  k $\Omega$ , for a  $C$  of 0.01  $\mu$ F. Using an SU536 op-amp and resistances of 16 k $\Omega$ , 820  $\Omega$ , and 330 k $\Omega$  respectively, we obtain the response shown in Fig. 4.5, having  $f_0 = 1024$  Hz,  $Q = 9.3$  ( $B = 110$  Hz), and a gain of 8.8. The response is shown with a scale of 250 Hz/division.